

# Microprocessors Lab

## 3- PWM

Instructor: Dr. Mohsen Raji

Graders:

- Mohammad Hossein Hashemi
- Negin Shirvani

Shiraz University – Fall 2022

Based on the slides by:

- Hossein Dehghanipour
- Mohammad Hossein Allah Akbari



## PWM:


Pulse Width Modulator.

If we want to produce a voltage between 0-5 volts (ex: 2.5, 3, etc.), we have to use PWM in order to do so.

On **Arduino Mega**, we have **distinct set of pins** for PWM, but on **Arduino Uno**, the pins that have a “~”


symbol beside them in the **Digital section** perform the PWM task.

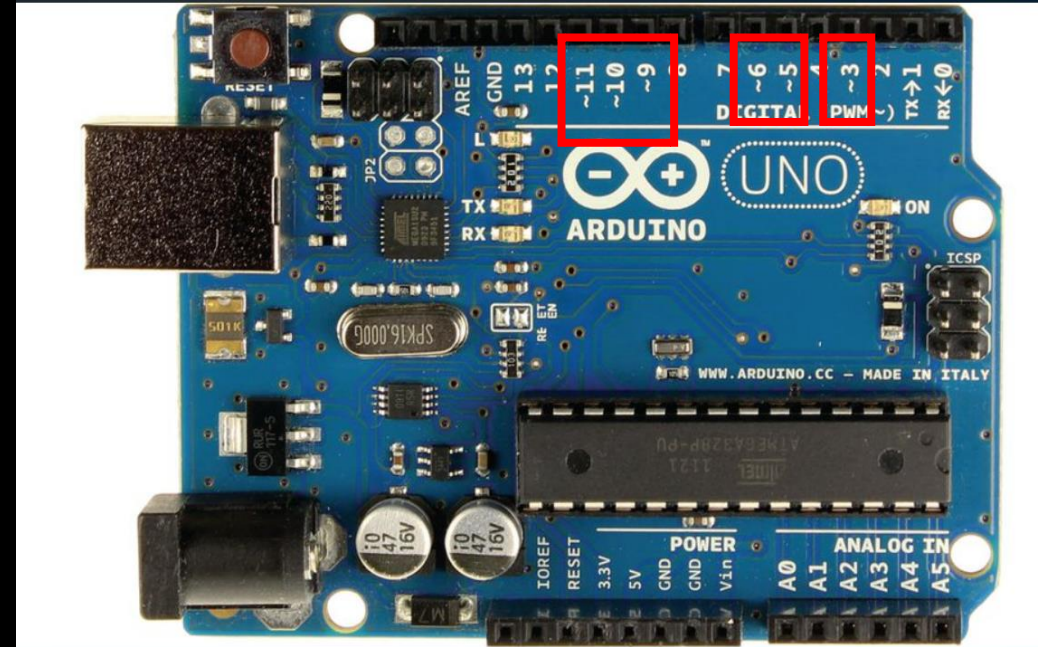Remember that you can use pins 0,1 on Arduino Mega as PWM if you are not using **Serial1**, **Serial2**, or **Serial3** instead.



Pins:  
3,5,6  
OR  
9,10,11


Pins 0-13

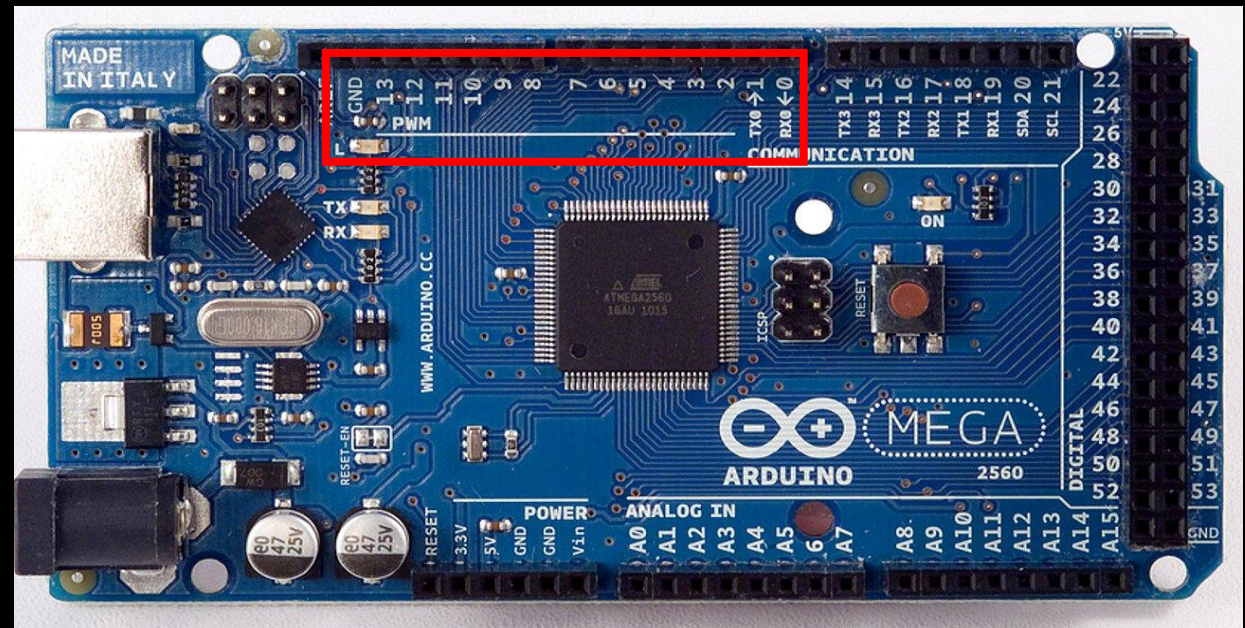
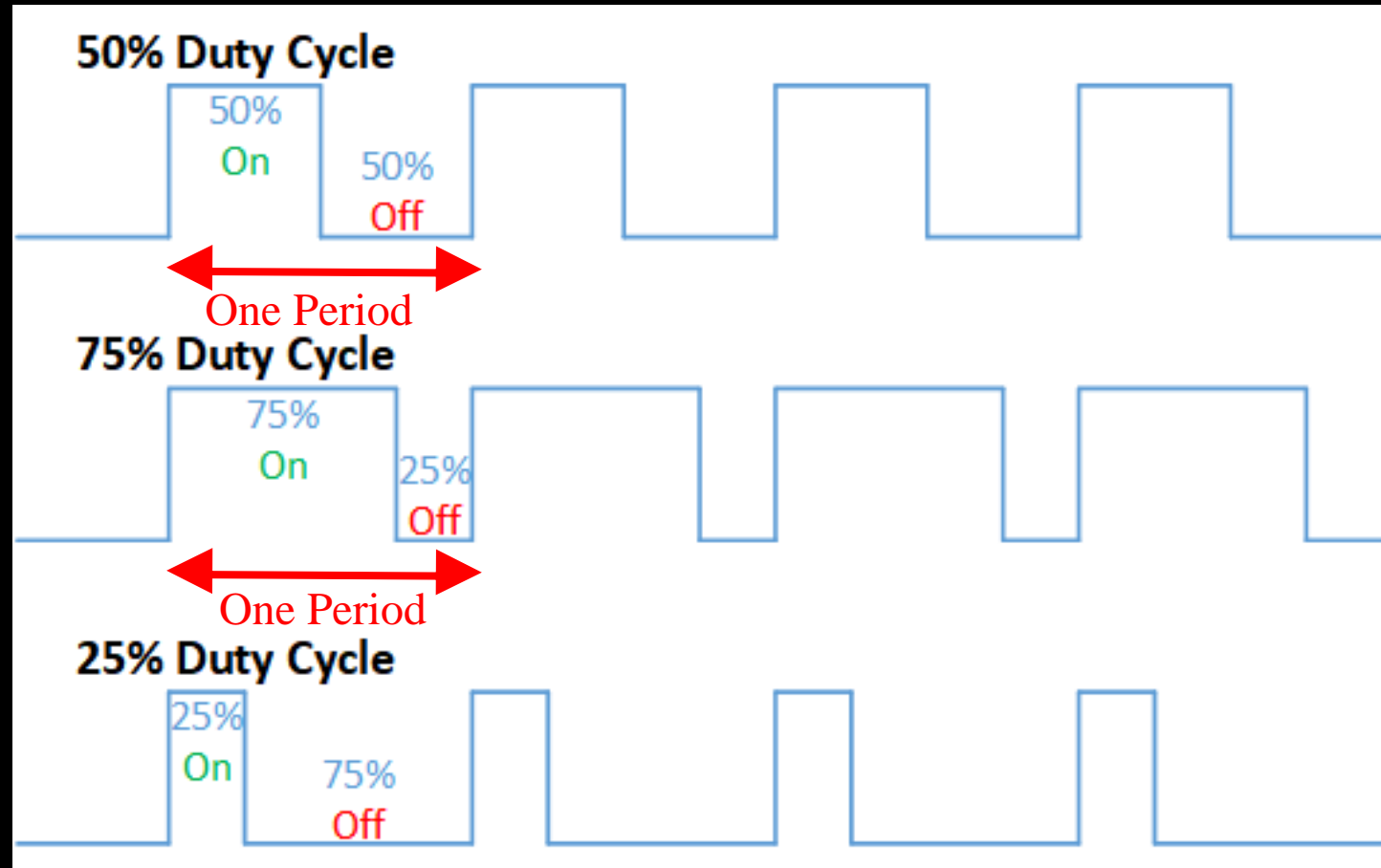
# Duty Cycle

You must be pretty much familiar with the concept of Duty Cycle (because you have studied it in the Micro Processor Course). The percentage of duty cycle determines the voltage of PWM. For example, if the duty cycle is **25%** and we are working with a board that can output **5V**, the voltage we are giving out from the PWM pin is  $25\% * 5 = 1.25$  volts.

$$\text{Duty Cycle} = \frac{\text{Period ON}}{\text{One Period}}$$



# Sample 1:


Test the following code on the given circuit.

```
#include <Arduino.h>

int LED = 9;

void setup() {
  // put your setup code here, to run once:
  pinMode(LED, OUTPUT);
}




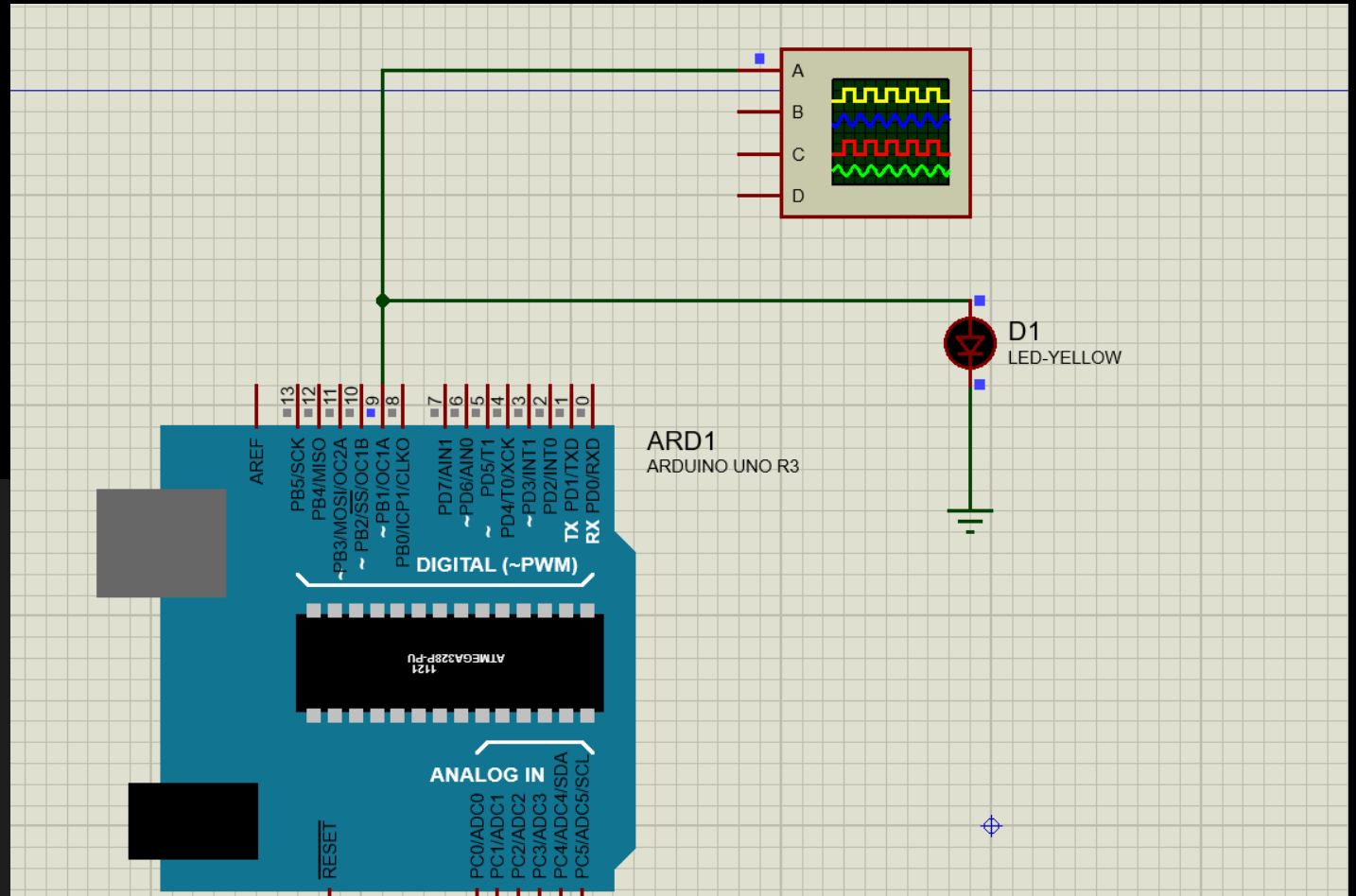
void loop() {
  // put your main code here, to run repeatedly:
  for (int i = 0 ; i < 256 ; i += 5){
    analogWrite(LED,i); // We use this function to write on Analog Pins.
    delay(100); //This function is used to let us see the difference better.
  }
}
```



**Question:**

Why should the loop go until 255? Can we exceed 255 for PWM? Why?

# *Output:*

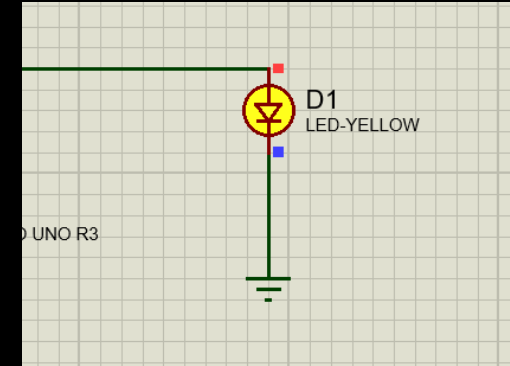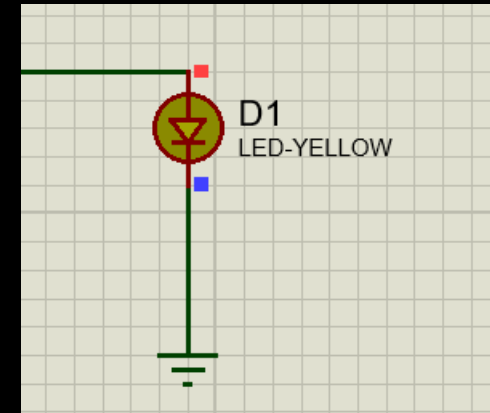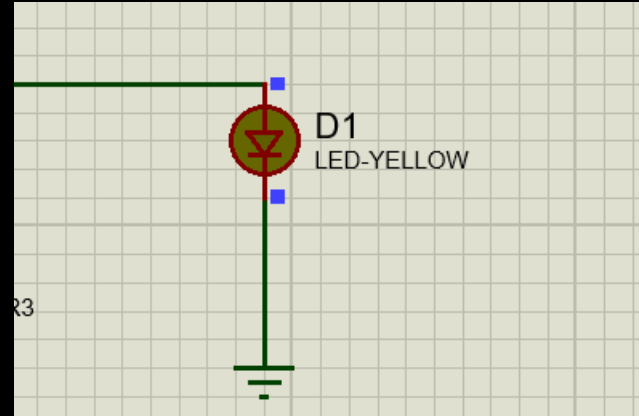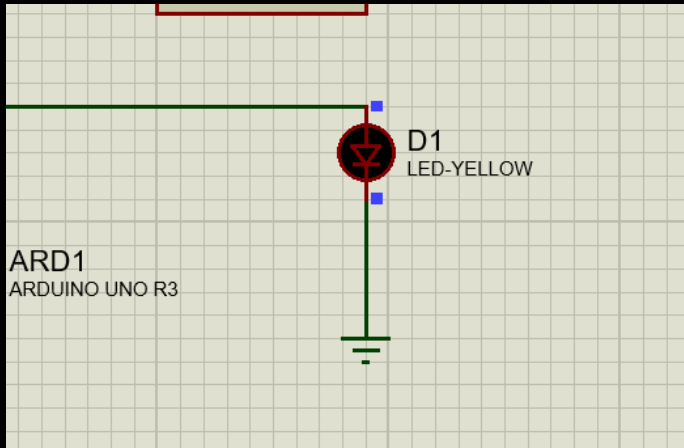

## Start

**Remember:**

In order to see the **analog signal (waves)** better, we use an Oscilloscope, Which can be seen on the top of the design on the previous slide.





- A **potentiometer** is a three-terminal resistor with a sliding or rotating contact that forms an adjustable voltage divider. If only two terminals are used, one end and the wiper, it acts as a **variable resistor** or **rheostat**.
- Reference: [Wikipedia](#)


We use potentiometer to change the input voltage from 0-5 volts. It is clear that this device gives us an analog signal and we have to use PWM unit to determines its given value.

# Sample 2:
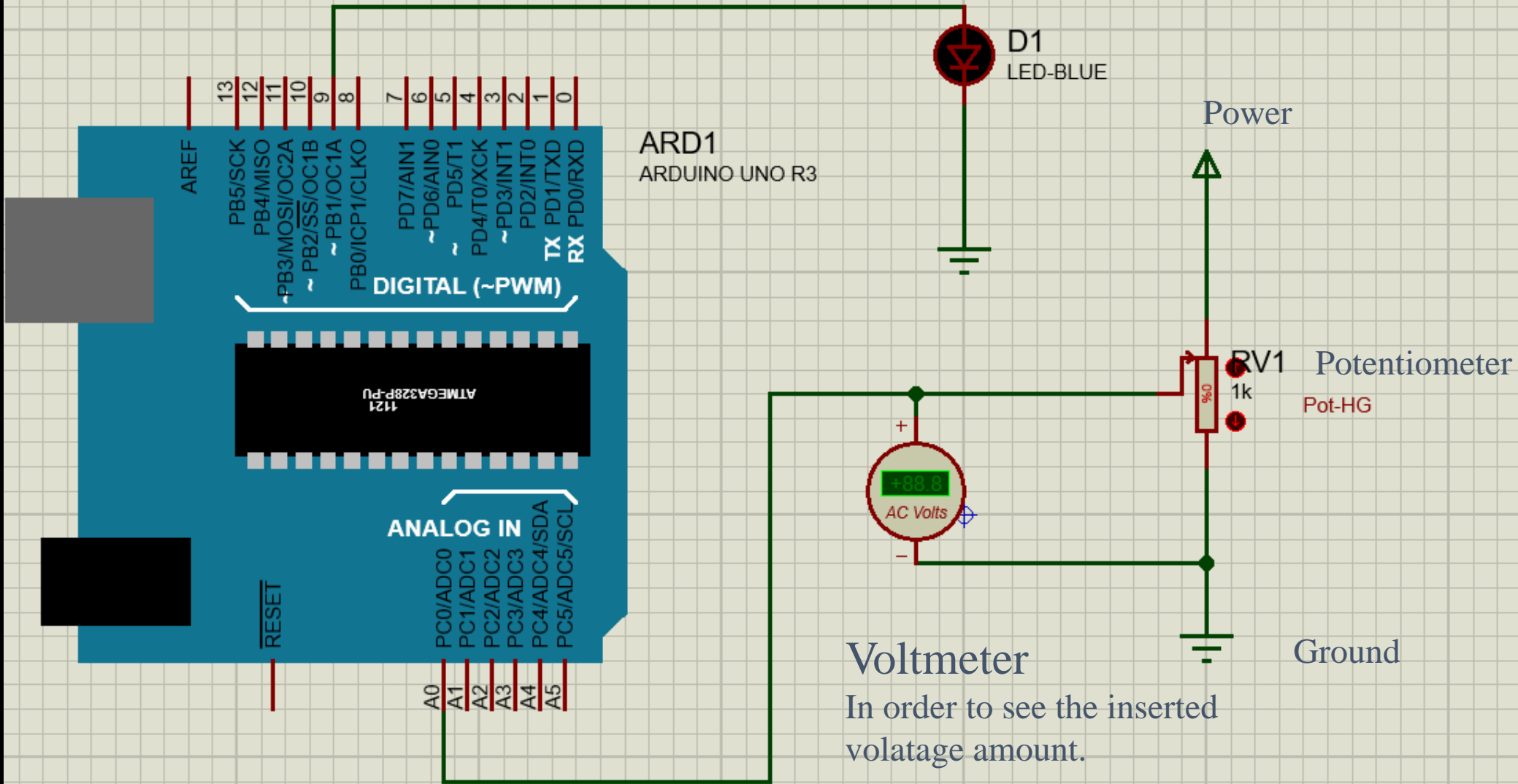
## Question:

Why should we divide the output of `analogRead()` by 4?




```
1  #include <Arduino.h>
2
3  int LED = 9 ;
4  int Potentiometer = A0 ;
5  int value = 0 ;
6
7
8  void setup() {
9      // put your setup code here, to run once:
10     pinMode(LED,OUTPUT);
11     pinMode(Potentiometer, INPUT);
12 }
13
14 void loop() {
15     // put your main code here, to run repeatedly:
16     value = analogRead(Potentiometer)/4 ;
17     analogWrite(LED,value);
18
19 }
20
```







Voltmeter

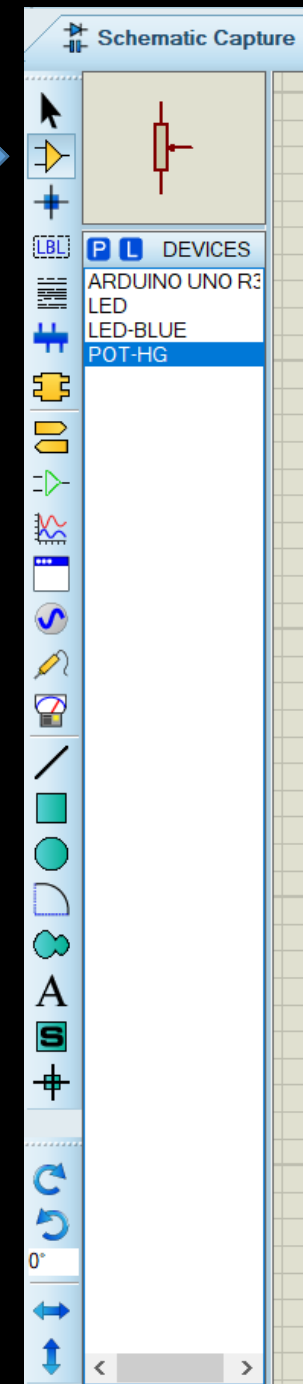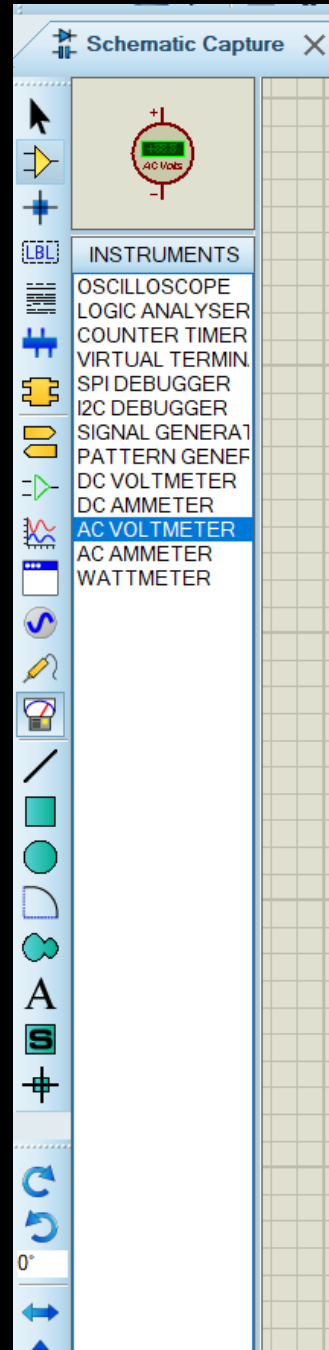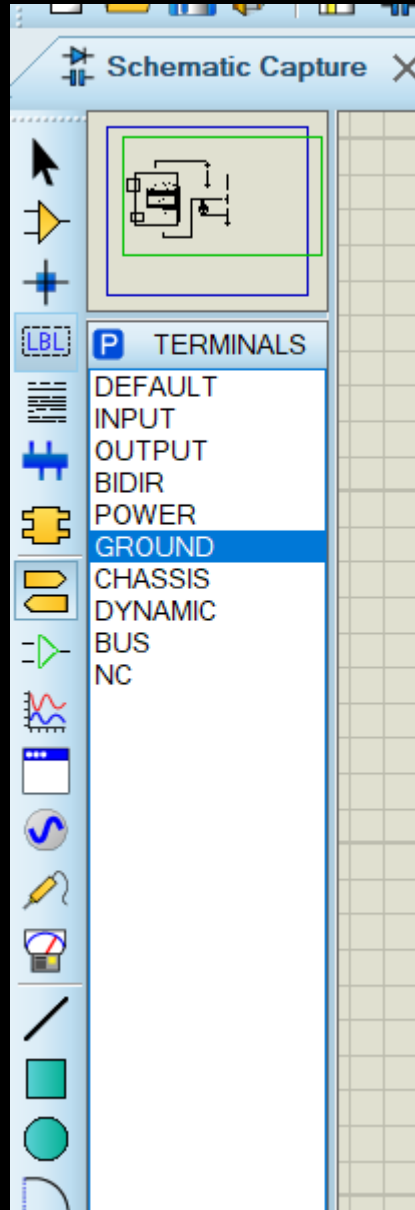In order to see the inserted  
volatage amount.





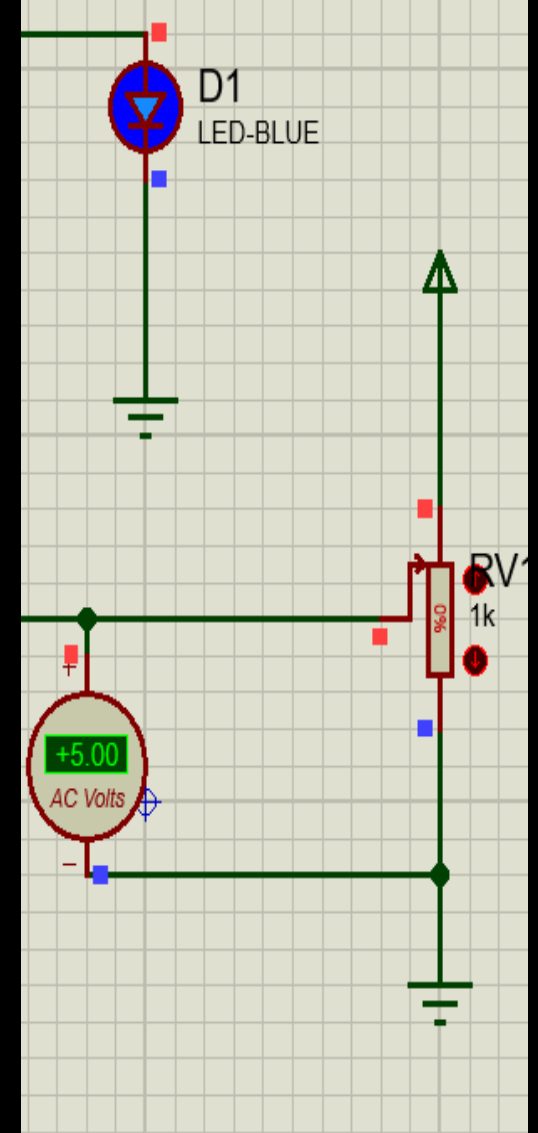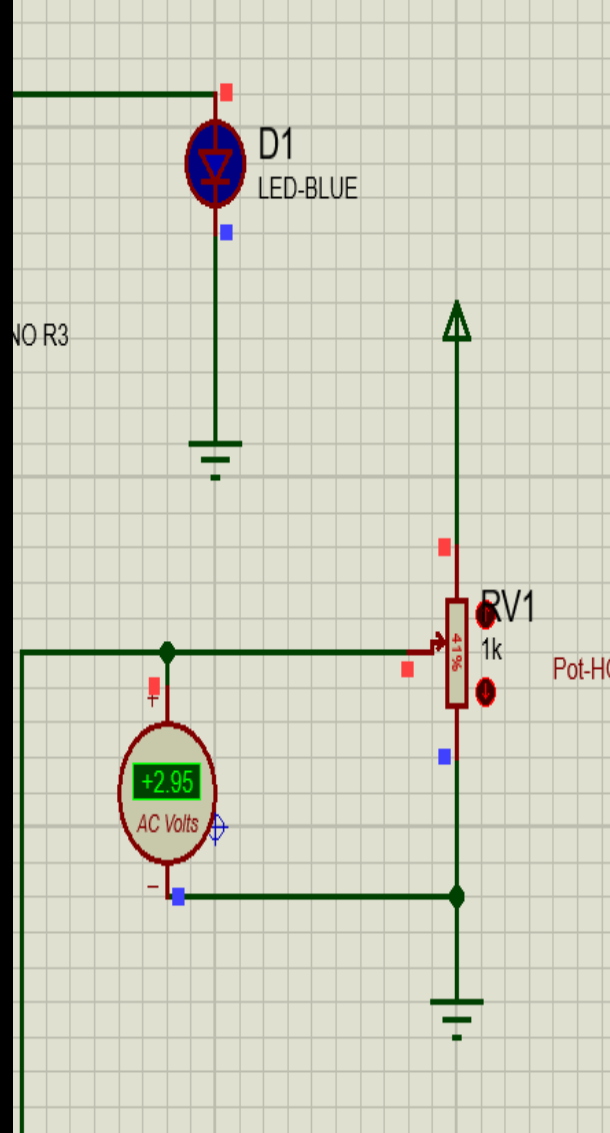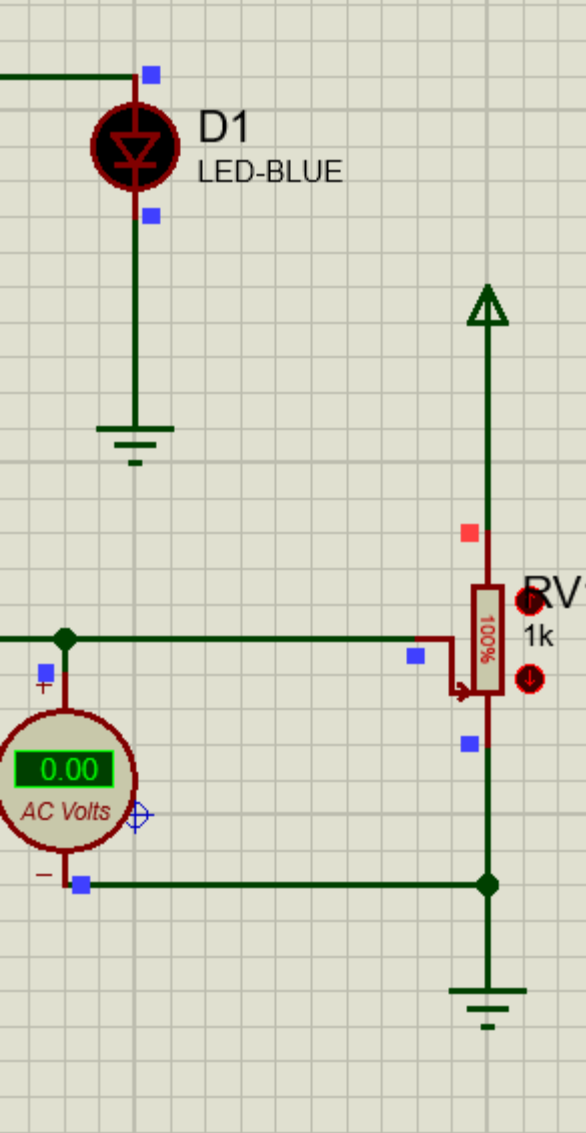

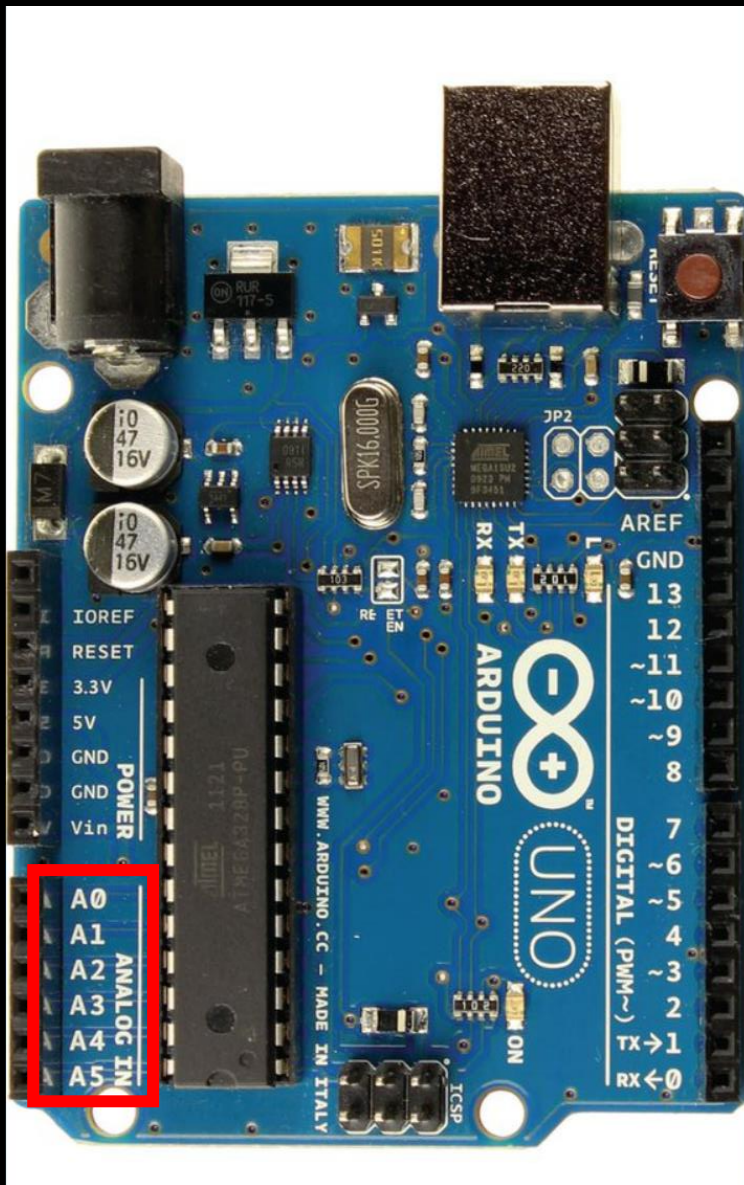

- Information inside our boards and chipsets are transferred in **digital** (0 & 1) format. On the other hand, **actuators** (motors, sensors, etc.) with **analog** (waves) format. In order to have these peripherals work with our chipsets, we use something called **ADC** (Analog to Digital Converter) and **DAC** (Digital to Analog Converter). These units work with the **Analog pins** that are on our board.



# Class Work I:

*Q.* Make a circuit, in which, you read data from 3 potentiometers and based on what the values are, turn a **RGB** LED.

You don't know how to work with RGB LED? [See HERE](#)

---

- Why don't we just connect heavy loads directly to Arduino board?

The answer is simple: **Current limitations** on Arduino **pins**! According to its datasheet each pin can at most deliver **40mA** and the total amount of current drawn from **all pins** shouldn't exceed **200mA in total** or the board will **fry**!

- So what is the solution?!

This is where the **MOSFETs** comes into the play. The idea is to use an **external power supply** that can **deliver** enough power to the desired device and **control** it using a switch. You guessed it didn't you? The switch here is the MOSFET. Every **transistor** acts as a **switch** at its **saturation mode** and that's exactly what we want. We supply the load using the external power source and control it with the help of **MOSFET**.

Q. Wait a minute; if all transistors can act as a switch, then, what's with all these insist on using MOSFET?

A. Actually that's a good question and you're going to answer it along with the rest of your homework.

---

## Class Work II:

**Q.** Control the RPM of a DC motor using Arduino and a potentiometer. The motor should be **supplied** using proper supply and the **switching** should be done with the help of and N-channel MOSFET with part number IRFZ44N.

**NOTE:** If you power the motor using Arduino your assignment won't be graded :). Arduino only assigns the RPM of the motor.

**Q.** Why are we insisting on **MOSFET** as our switch? Why don't we use any type of transistor?

---



# If you had any questions:

1. Google is your friend!
  2. If you did not find your answer on Google, search it on YouTube. There is definitely an Indian fellow answering your questions.
  3. After all, you can also ask your graders (:
-